

Name:- Lakshman Mulchandani

Roll no.:- 20117048

Branch:- Electrical Engineering

PAGE NO.:


DATE

Assignment -2

Conversion of h parameters in transistor three configurations

Common Base

Circuit of redrawn CB configuration

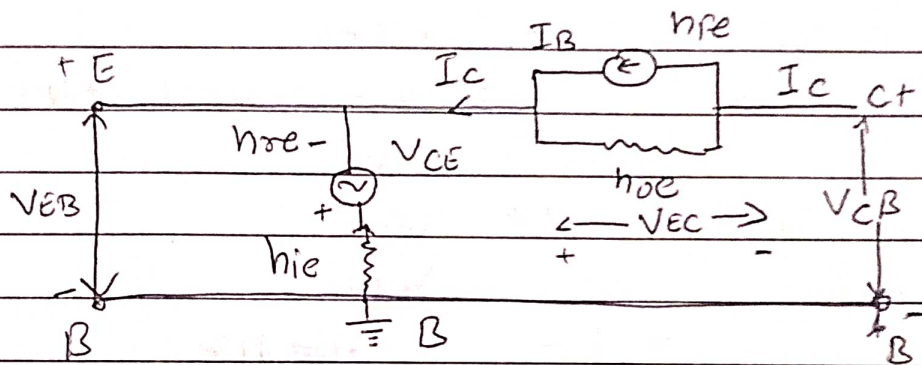

By definition

$$h_{re} = \frac{V_{eb}}{V_{cb}} = \frac{V_{ec} + V_{cb}}{V_{cb}}$$

$$h_{re} = 1 + \frac{V_{ec}}{V_{cb}}$$

$$\text{If } I_e = 0, \quad I_c = -I_B$$

$$\therefore I_c = h_{fe} I_B - h_{oe} V_{ec}$$

$$-I_B = h_{fe} I_B - h_{oe} V_{ec}$$

$$h_{oe} V_{ec} = (1 + h_{fe}) I_B$$

Applying KVL at output mesh

$$h_{ie} I_B + h_{re} V_{ce} + V_{ec} + V_{cb} = 0$$

$$h_{ie} \left(\frac{h_{oe} V_{ec}}{1 + h_{fe}} \right) - h_{re} V_{ec} + V_{ec} + V_{cb} = 0$$

$$\frac{h_{ie} h_{oe}}{1 + h_{fe}} + (1 - h_{re})(1 + h_{fe}) \cdot V_{ec} = -V_{cb}$$

$$\frac{V_{ec}}{V_{cb}} = \frac{-(1 + h_{fe})}{h_{ie} h_{oe} + (1 - h_{re})(1 + h_{fe})}$$

$$\begin{aligned} \therefore h_{rb} &= 1 + \frac{V_{ec}}{V_{cb}} \\ &= 1 - \frac{1 + h_{fe} h_{re}}{h_{ie} h_{oe} + (1 - h_{re})(1 + h_{fe})} \end{aligned}$$

$$h_{rb} = \frac{h_{ie} h_{oe} - h_{re}(1 + h_{fe})}{h_{ie} h_{oe} + (1 - h_{re})(1 + h_{fe})}$$

$$\therefore h_{re} \ll 1 \text{ and } h_{ie} h_{oe} \ll 1 + h_{fe}$$

$h_{rb} = \frac{h_{ie} h_{oe}}{1 + h_{fe}} - h_{re}$
--

By definition,

$$h_{ob} = \frac{I_c}{V_{cb}} = \frac{-I_B}{V_{cb}}$$


By definition,

$$\begin{aligned}
 h_{ob} &= \frac{I_c}{V_{cb}} = \frac{-I_B}{V_{cb}} \\
 &= \frac{-I_B (1 + h_{fe})}{(h_{ie} h_{oe} + (1 - h_{re})(1 + h_{fe})) V_{ce}} \\
 &= \frac{1 + h_{fe}}{h_{ie} h_{oe} + (1 - h_{re})(1 + h_{fe})} h_{oe} \\
 &= \frac{h_{oe}}{h_{ie} h_{oe} + (1 - h_{re})(1 + h_{fe})}
 \end{aligned}$$

∴ $h_{re} \ll 1$ and $h_{ie} h_{oe} \ll 1 + h_{fe}$

$$h_{ob} \approx \frac{h_{oe}}{1 + h_{fe}}$$

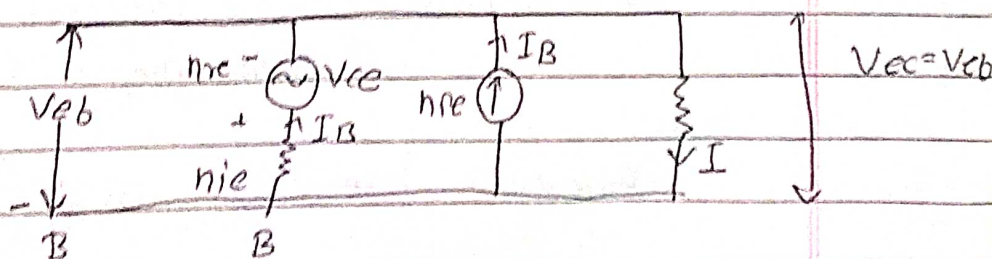If terminals C and B are connected,
 $V_{ec} = V_{eb}$



Applying KVL at input mesh,

$$V_{eb} + h_{re} V_{ce} + h_{ie} I_b = 0$$

$$V_{eb} - h_{re} V_{ec} + h_{ie} I_b = 0$$

$$I_b = - \frac{(1 - h_{re}) V_{eb}}{h_{ie}}$$

Applying KCL at node:

$$I_b + I_e + h_{fe} I_b - h_{oe} V_{eb} = 0$$

$$I_e = - (1 + h_{fe}) I_b + h_{oe} V_{eb}$$

$$I_e = V_{eb} \left[h_{oe} + \frac{(1 + h_{fe})(1 - h_{re})}{h_{ie}} \right]$$

By definition,

$$h_{ib} = \frac{V_{eb}}{I_e}$$

$$= \frac{h_{ie}}{h_{oe} h_{ie} + (1 - h_{re})(1 + h_{fe})}$$

since, $h_{re} \ll 1$ and $h_{oe} h_{ie} \ll 1 + h_{fe}$

$$h_{ib} = \frac{h_{ie}}{1 + h_{fe}}$$

By definition,

$$h_{fb} = \frac{i_e}{i_b}$$


$$= \frac{V_{eb} \left(\frac{-h_{re}(1-h_{re}) - h_{ie}h_{oe}}{h_{ie}} \right)}{V_{eb} \left(\frac{h_{ie}h_{oe} + (1-h_{re})(1+h_{re})}{h_{ie}} \right)}$$

$$= - \left(\frac{h_{ie}h_{oe} + (1-h_{re})h_{re}}{h_{ie}h_{oe} + (1-h_{re})(1+h_{re})} \right)$$

$$\because h_{re} \ll 1 \quad \text{and} \quad h_{ie}h_{oe} \ll 1+h_{re}$$

$$h_{fb} = - \frac{h_{re}}{1+h_{re}}$$

Common Collector configuration

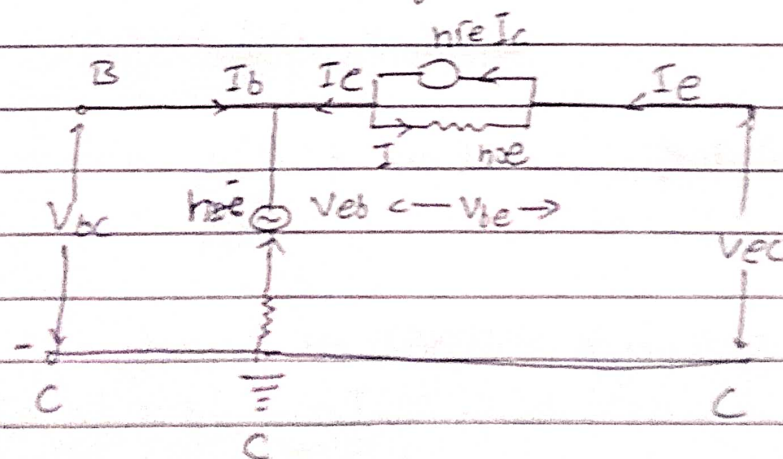

By definition,

$$h_{rc} = \frac{V_{be}}{V_{ce}} = \frac{V_{be} + V_{ce}}{V_{ce}}$$

$$= 1 + \frac{V_{be}}{V_{ce}} = 1 - \frac{V_{be}}{V_{ce}}$$

~

$$h_{re} = 1 - h_{fe}$$

since $I_b = 0$,
 $I_e = -I_c$

$$h_{oc} = \frac{-I_c}{V_{ec}} = \frac{I_c}{V_{ce}}$$

$$h_{oc} = h_{oe}$$

If terminals C and E are connected,

$$V_{ce} = V_{bc}$$

$$h_{ic} = \frac{V_{bc}}{I_b} = \frac{V_{be}}{I_b}$$

$$h_{ic} = h_{ie}$$

since, $h_{fe} = \frac{I_e}{I_b}$

applying KCL at node,

$$I_e + I_b + I_c = 0$$

$$I_e = -(I_b + I_c)$$

$$h_{fe} = \frac{-I_b + I_c}{I_b}$$

$$= -\left(1 + \frac{I_c}{I_b}\right)$$

since, $\frac{I_c}{I_b} = h_{fe}$

